

CIM



B11901027 王仁軒


Outline

- Analog vs Digital
- Analog CIM structure
 - Optimization techniques for analog designs
- Digital CIM structure
 - Optimization techniques for digital designs
- Overall comparison among 3 papers

Analog CIM Structure


□ Typical analog CIM Structure

- Require DAC & ADC

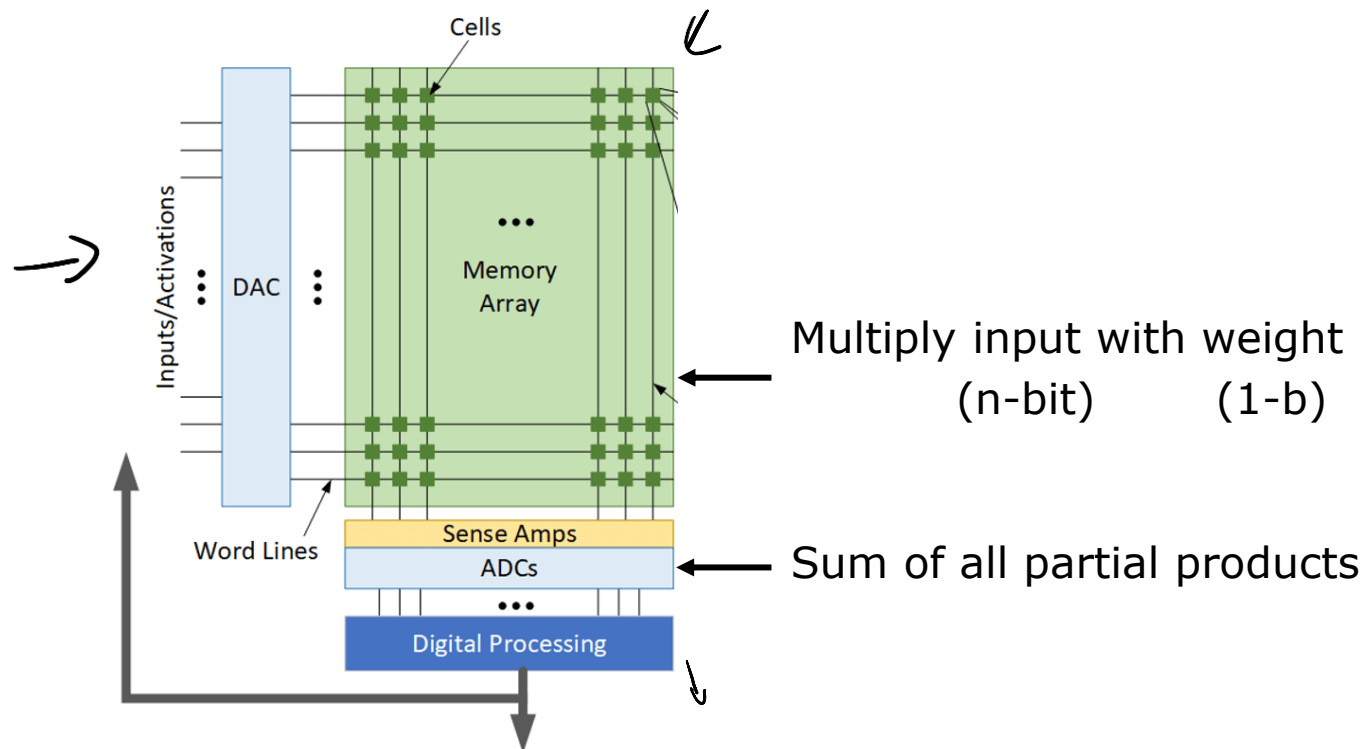


Optimization for Analog Designs

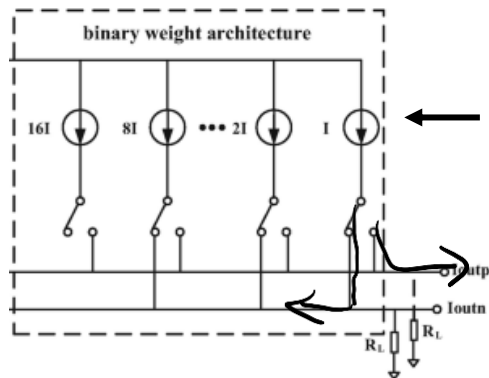- ❑ Analog multiplication requires DAC
 - Current source may consume lots of power




Differential output
Current source are always on

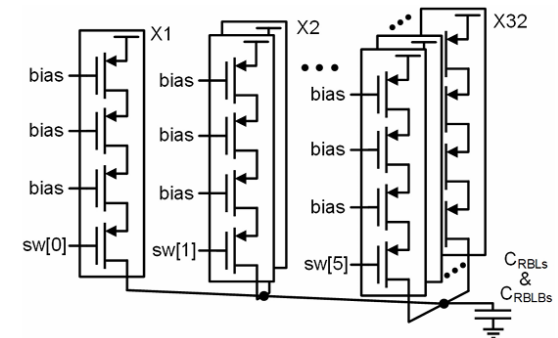Single-ended output
Can turn off current source



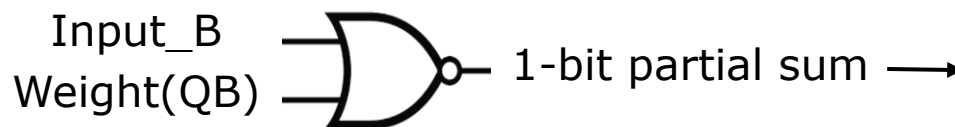- ❑ Not using DAC
 - Digital multiplication




Require shift and sum
to do n-bit x n-bit
from 1-bit x 1-bit

$$4b \times 4b \rightarrow 16$$


Optimization for Analog Designs

□ ADC is required

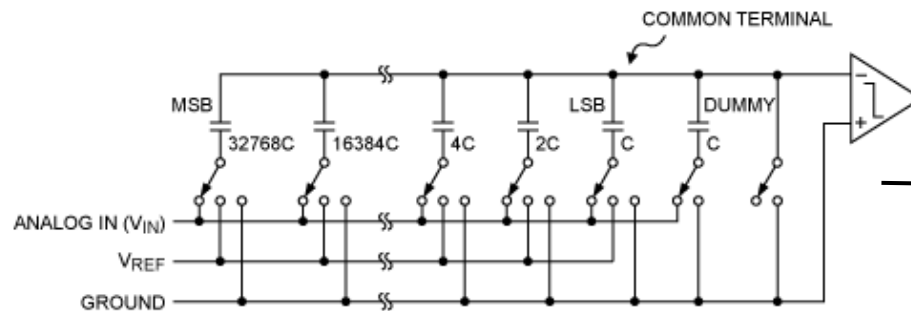

Capacitance $\propto 2^{\text{Bit precision}}$
Large area for caps


□ Reuse of Capacitors

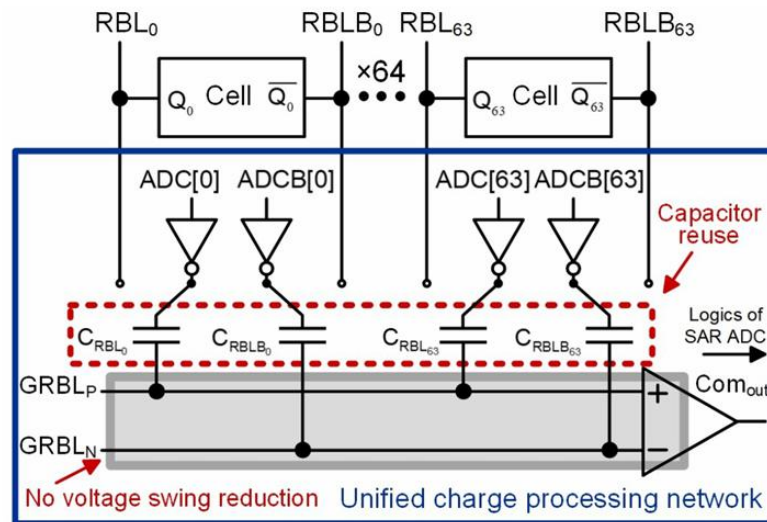

Reuse of caps for ADC
allows us to save area

Optimization for Analog Designs

❑ Skipping iterations

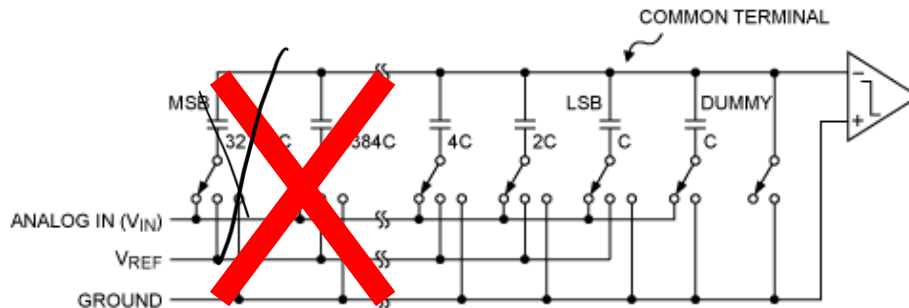

26


127

Input has 32 1's


Partial sum < 32

Skip first few iterations
saves time

❑ Interleaving (memory cell)

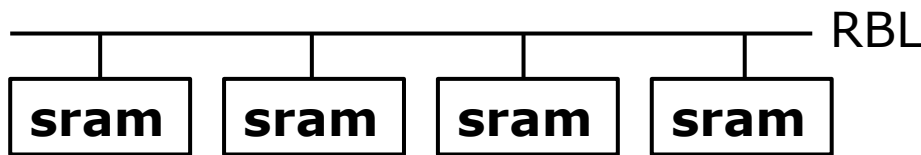

RBL length = L
Parasitic caps = C

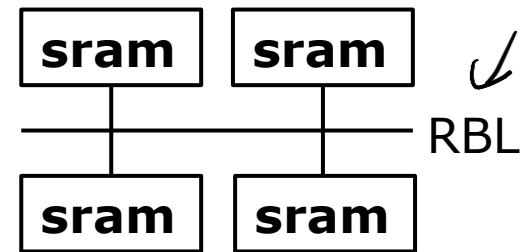


RBL length = L/2
Parasitic caps = C/2

256 C
256 C

Digital CIM Structure

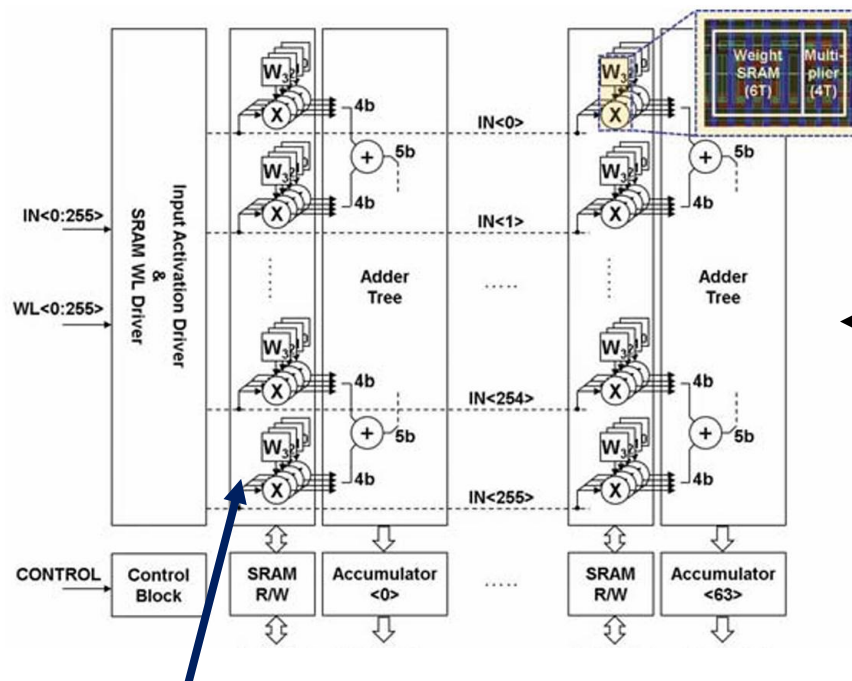- Typical digital CIM design
 - Serial input




Digital multiplication
(1b input x 4b weight)

← Adder tree to sum
all partial sums


Optimization for Digital Designs

□ Increase throughput

■ Increase input BW

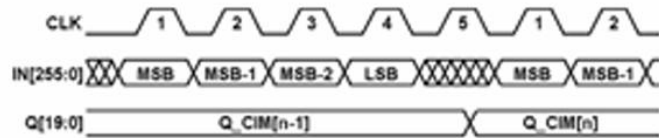




Require bit-precision+1 cycles

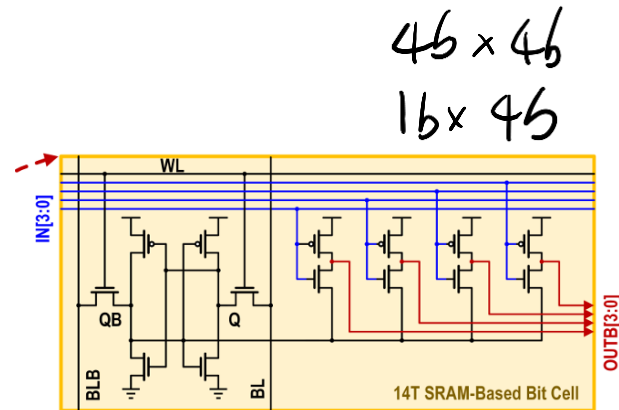

Require bit-precision/4+1 cycles

□ High BW input memory


■ In order to support MAC pipeline

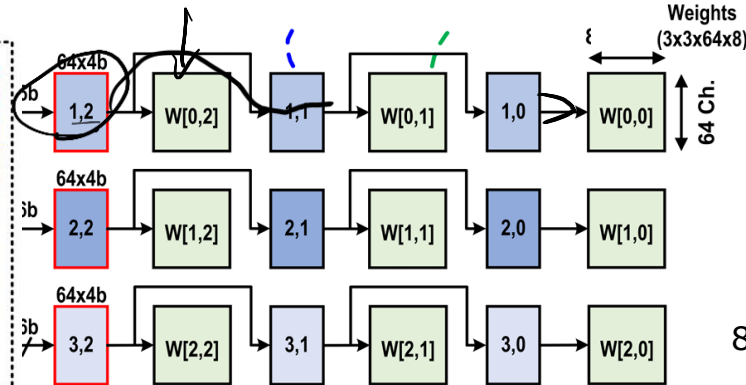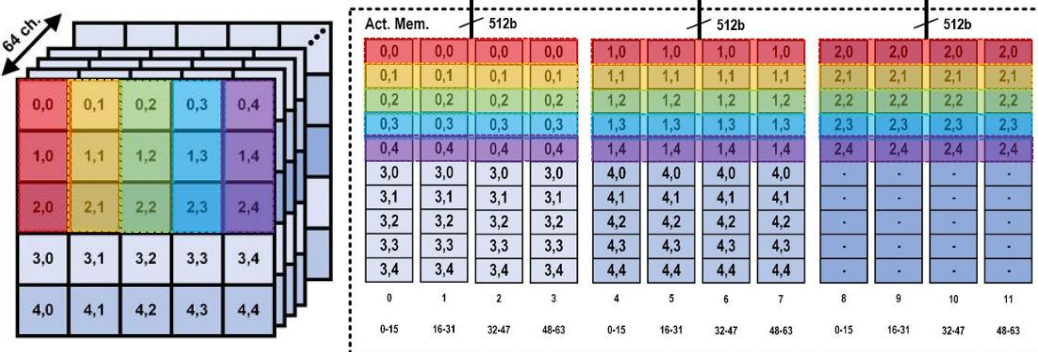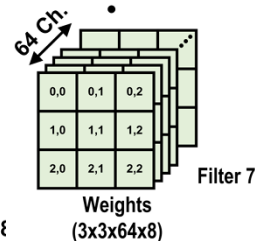

Optimization for Digital Designs

Bit-flexibility & Adder tree optimization

FA $3\ 1b \rightarrow 2\ 1b$

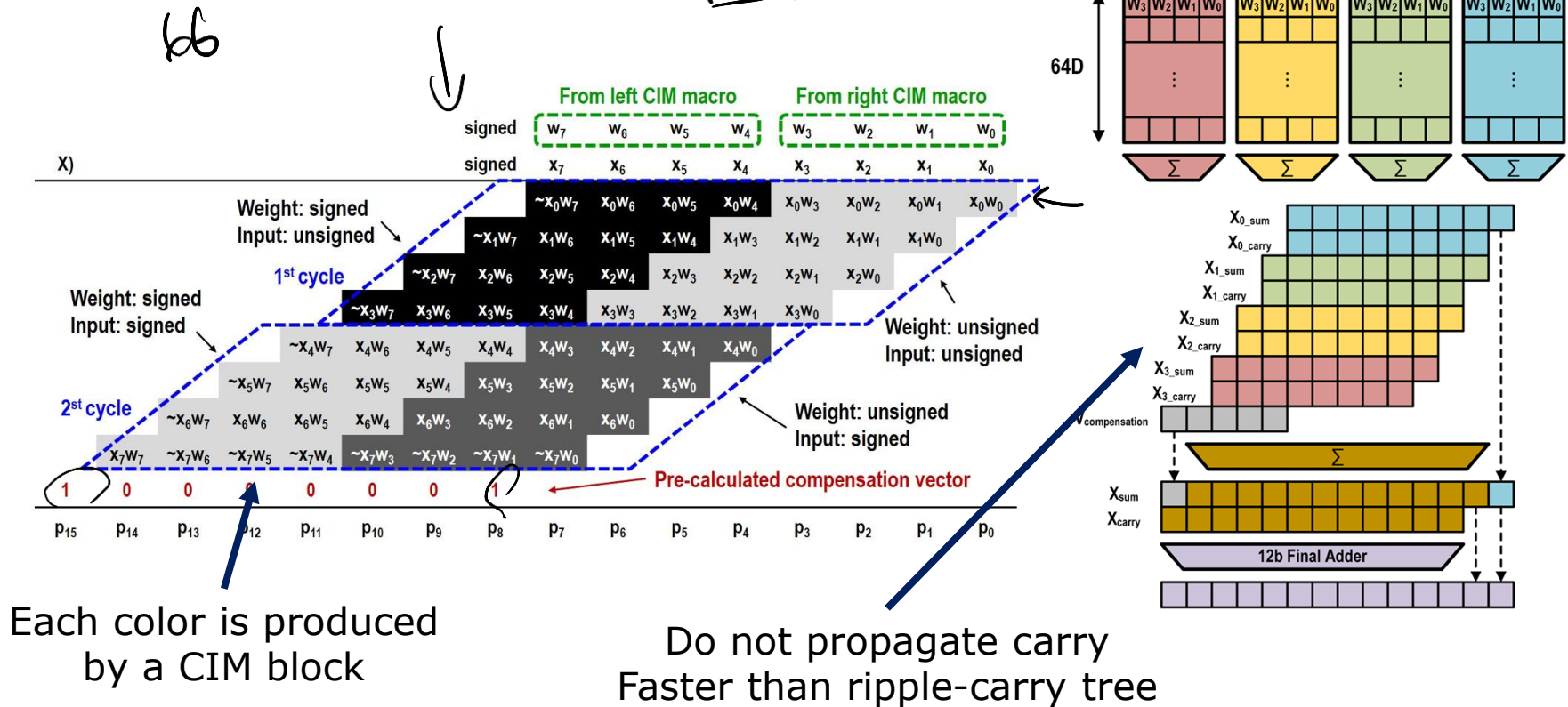

Overall Comparison

	2021/Analog	2023/Analog	2022/Digital
Throughput TOPS (1b x 1b)	Cycle time ↑ 1.30 7b x 1b	1.31 1b x 1b	98.3 4x4 MAC + Adder
Energy Efficiency TOPS/W (1b x 1b)	293	291	625
Area Efficiency TOPS/mm ² (1b x 1b)	23.01	27.7	10.49