Noise Margin


B11901027 王仁軒

Procedure

- Hspice simulation
- Download data
- Post-processing done by python
 - Rotate the curves ccw by 45 degree
 - Subtract two curves
 - Find min(local maximum, -local minimum) for SNM, RNM
 - Find local maximum (or global maximum) for WNM

SNM (corners)


■ Best at SF, worst at FF

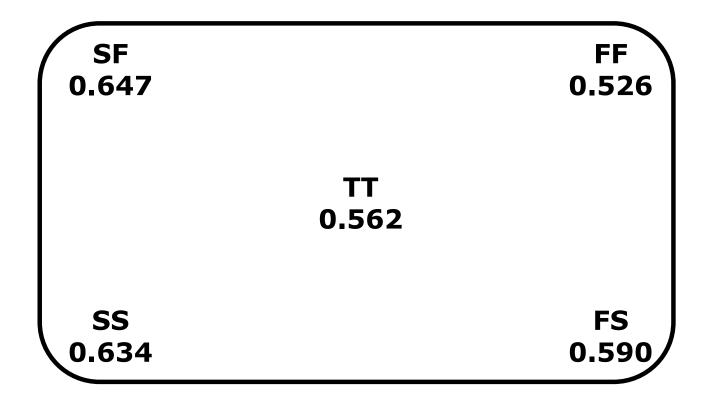

SNM (supply voltage)

- □ Roughly linear to VDD
 - At TT



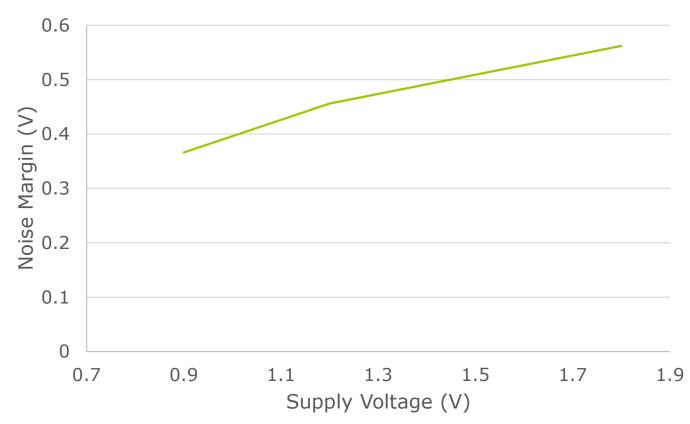

SNM (width)

- Noise margin ↑ with Wn ↓ or Wp ↑
 - VDD = 1.8 V


0.564

Wp = 0.25 um

0.533

RNM (corners)

■ Best at SF, worst at FF

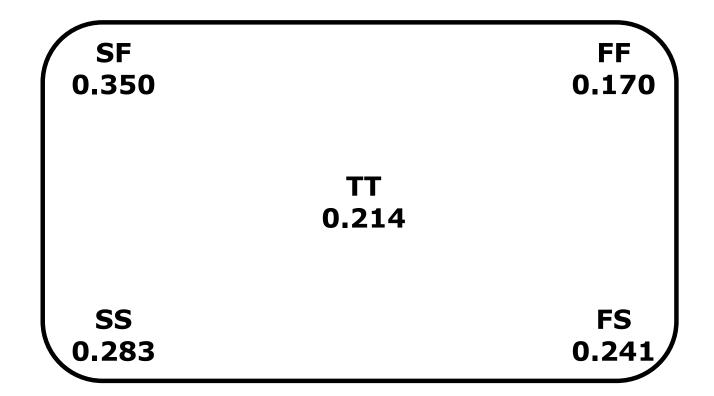


RNM (supply voltage)

□ NM ↓ with VDD ↓

At TT



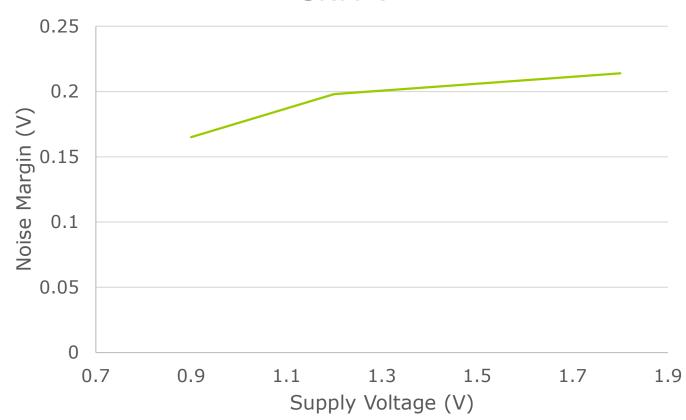


RNM (width)

- ■Noise margin ↑ with Wn ↓ or Wp ↑
 - VDD = 1.8 V

Wn =
$$0.60 \text{ um}$$
 Wn = 0.72 um Wn = 0.84 um 0.167 0.214 0.237

WNM (corners)


■ Best at FF, worst at FS

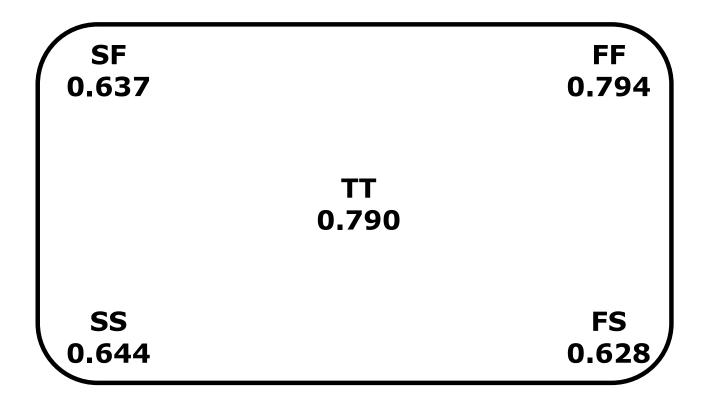

WNM (supply voltage)

- □ Roughly linear to VDD
 - At TT



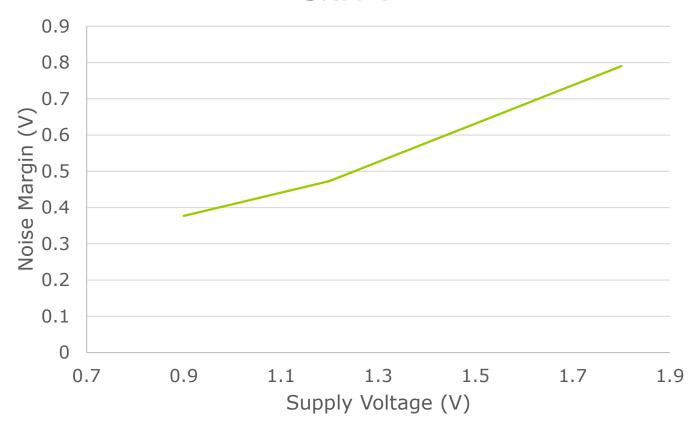



WNM (width)

- ■Noise margin ↑ with Wn ↓ or Wp ↑
 - VDD = 1.2 V

WNM

■Some special cases

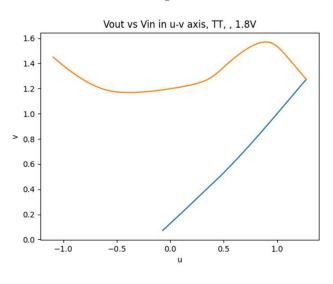

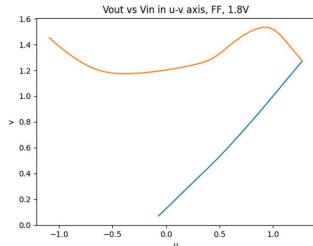

monotonic

