

Adder Tree / MAC



B11901027 王仁軒

Adder Tree Implementation



1st


2nd

3rd

4th

5th


6th

 

■ 28T FA
Wp 750n
Wn 250n

Adder Tree Result

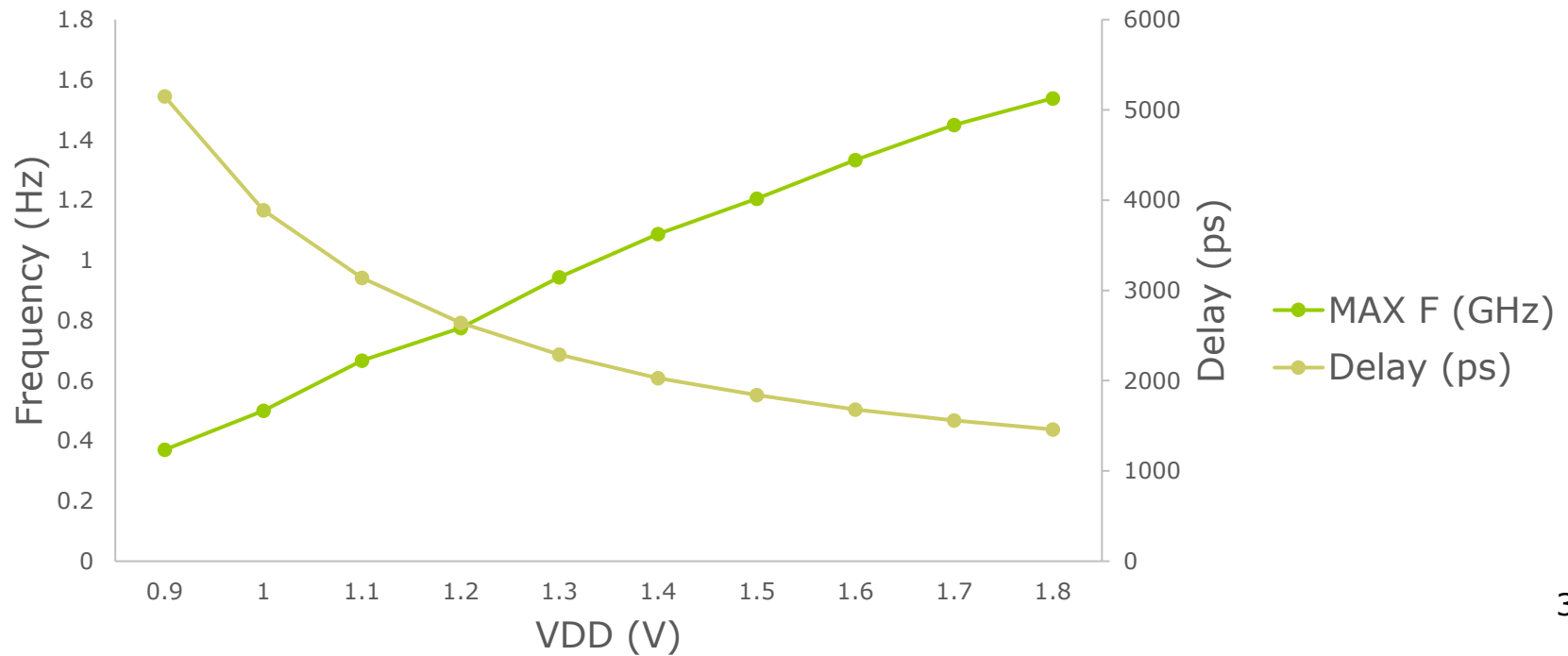
- Allowable clock rate grows with VDD
 - 0.37GHz at 0.9V, 1.54GHz at 1.8V
- Delay decreases with VDD growth
 - 5.15ns at 0.9V, 1.46ns at 1.8V



MAC Implementation


- N bit MAC has
N AND gate and
one adder tree
- 64 bit MAC composed of
one 32 bit MAC ,
two 16 bit MAC , and
some additional FAs

32 bit MAC

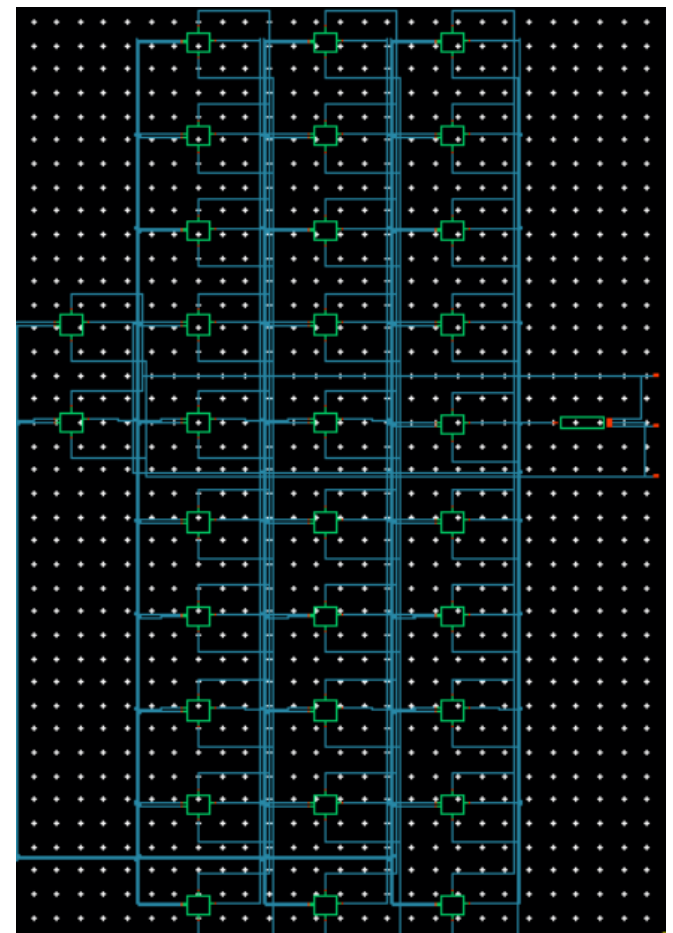



MAC Result

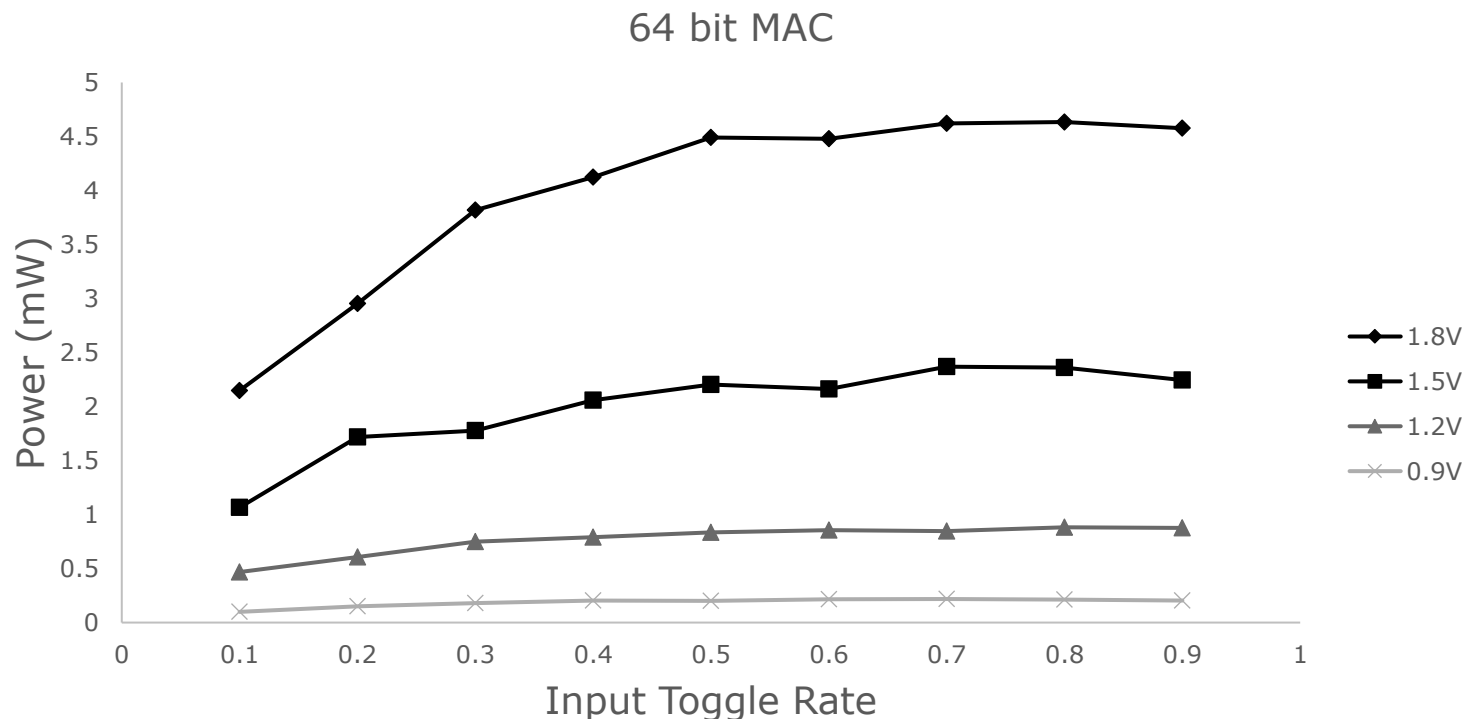- Dynamic power grows with toggle rate
 - But decreases when toggle rate 0.8 -> 0.9
 - Due to 50% 1s and 0s in test data



MAC Result

 
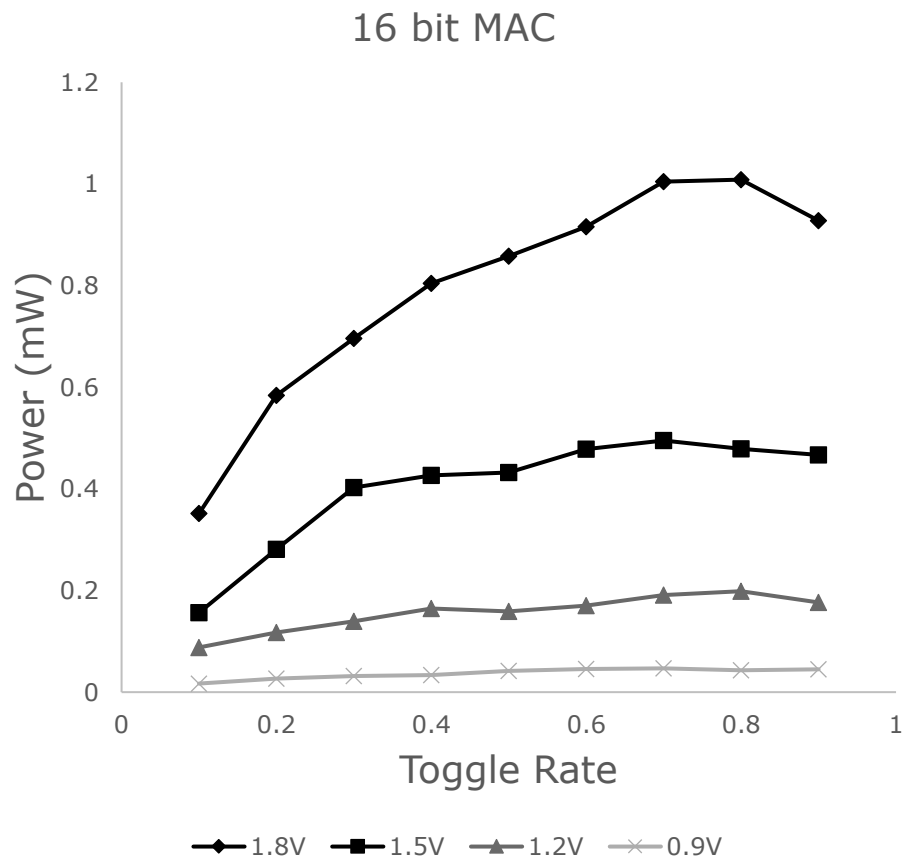
□ Same situation occurs for 16 and 32 bit MAC



MAC Result

□ Delay

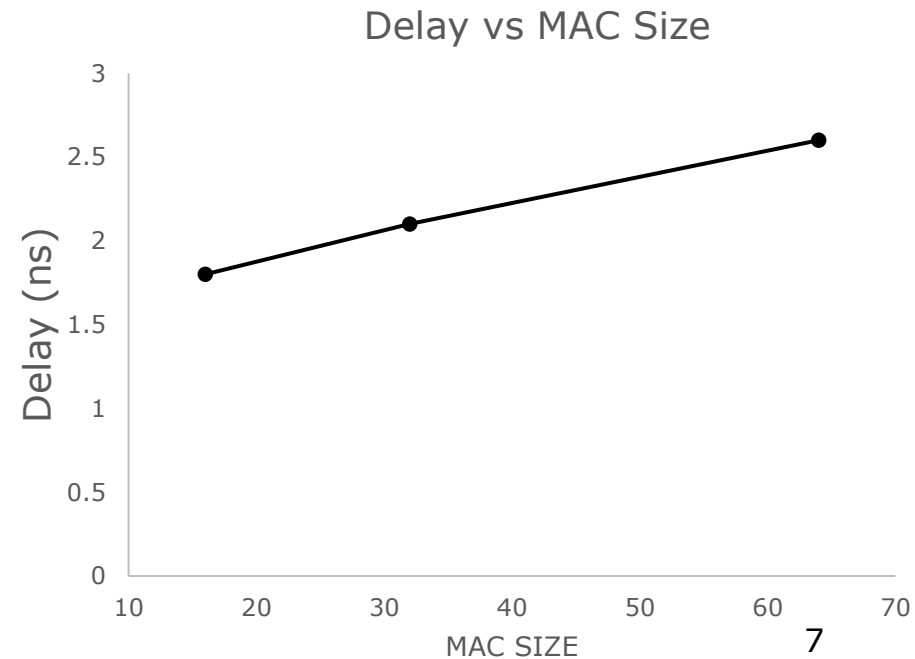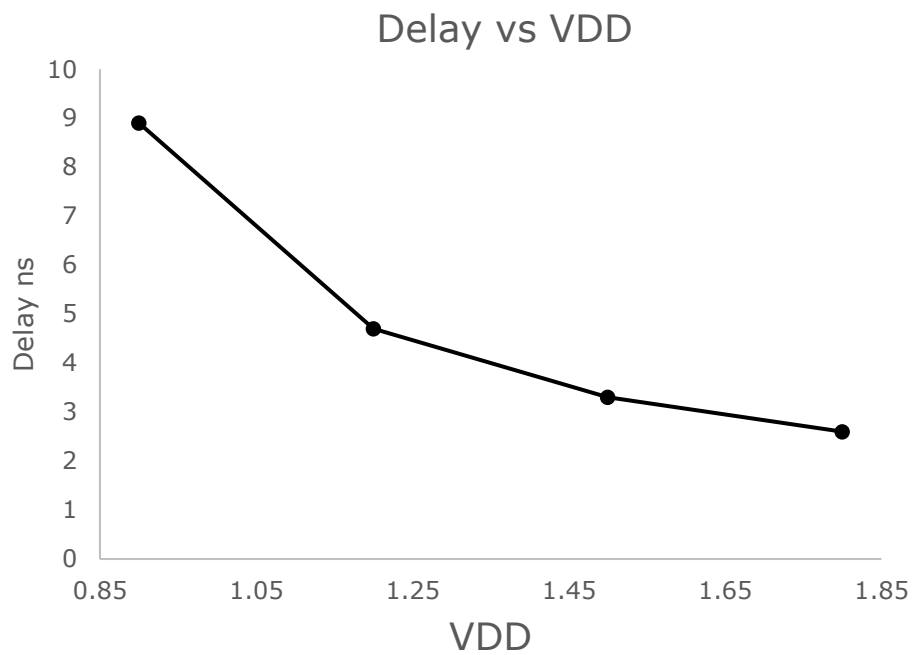■ 2.6 ns under 1.8 V, 8.9 ns under 0.9V supply



MAC Result


Energy efficiency

0.33 TOPS/W at 1.8V, 1.70 TOPS/W at 0.9V


Area efficiency

0.83 TOPS/mm² at 1.8V, 0.20 TOPS/mm² at 0.9V

Energy efficiency

 

Area efficiency

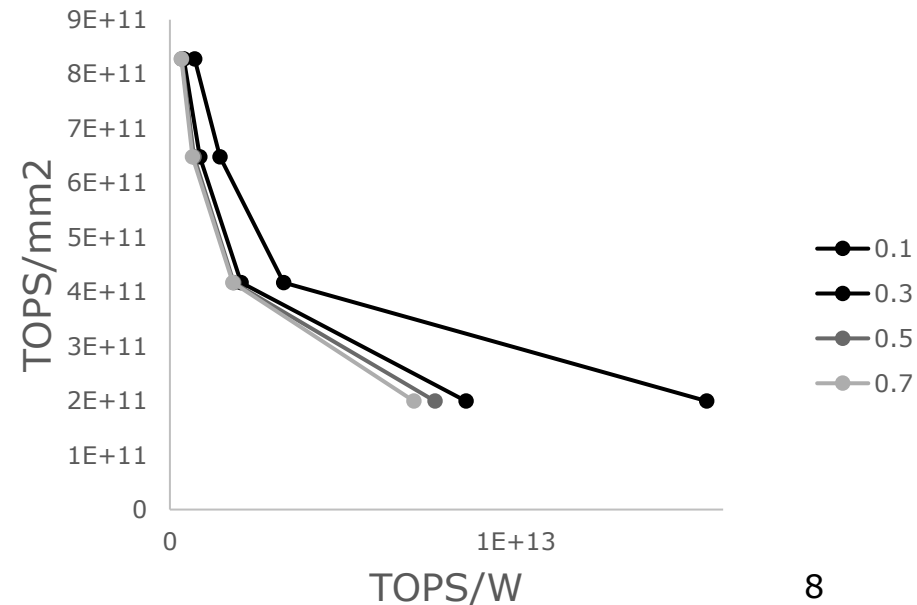

MAC Result


Energy efficiency

■ 4.38 TOPS/W for 16b, 0.72 TOPS/W for 64b

Area efficiency

■ 3.76 TOPS/mm² for 16b, 0.83 TOPS/mm² for 64b

Energy efficiency

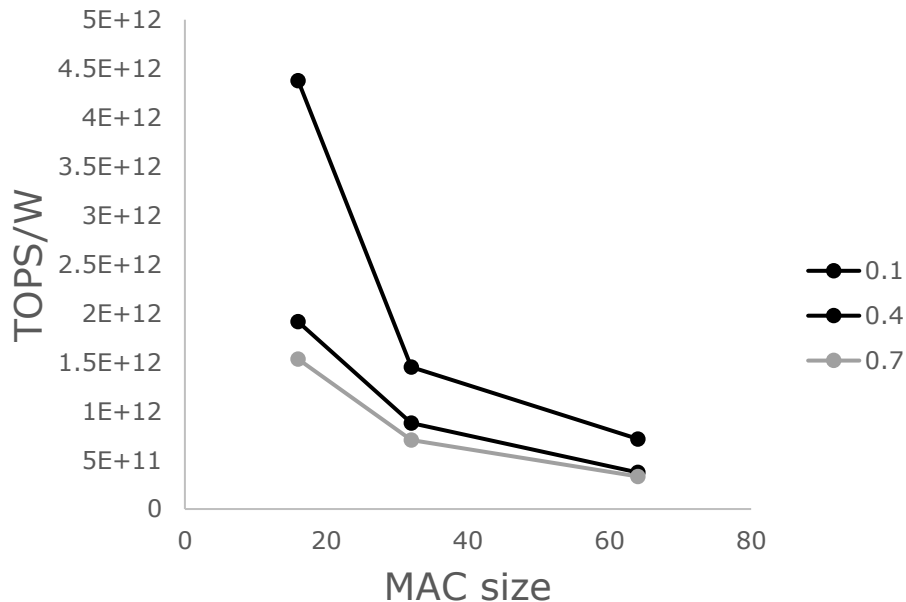

Area efficiency

