


2021



B11901027 王仁軒

Motivation & Background

 - ML computing is data-centric
 - Energy in Traditional Von Neumann structure is mainly consumed by memory accesses
 - Computation in memory tackles this problem
- CIM structures focus on analog approach more
 - Analog designs lack accuracy ($\text{SNR} \propto \frac{1}{\sqrt{\text{Bit}}}$)
 - Using digital structures can guarantee accuracy, also good for operations such as batch-norm, pooling




Features

- High bit-flexibility
 - Programmable bit-widths, signed/unsigned, and weights with 4, 8, 12, 16 bit widths..
- Parallel MAC operations, with high energy/area efficiency
- Allows simultaneous MAC and write operations
 - Time is wasted when updating weights

Structure

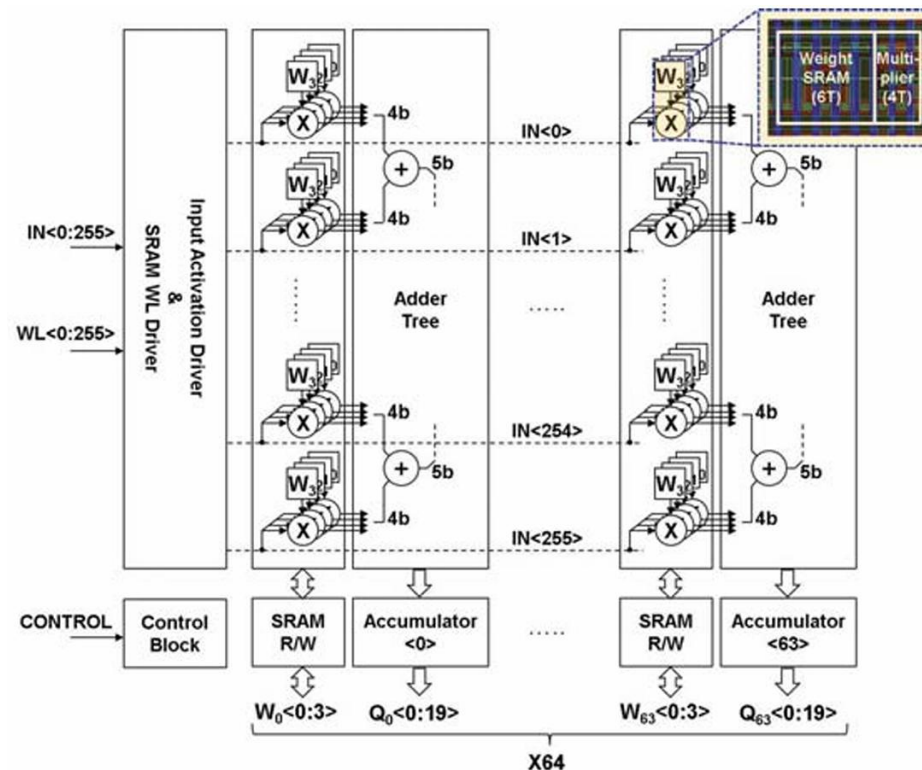- 2 Mode: SRAM & CIM
 - SRAM: update weight
 - CIM : MAC operation, support 256×64 multiplication





Structure

■ 2 Mode: SRAM & CIM

□ SRAM: update weight

□ CIM : MAC operation , support 256×64 multiplication

 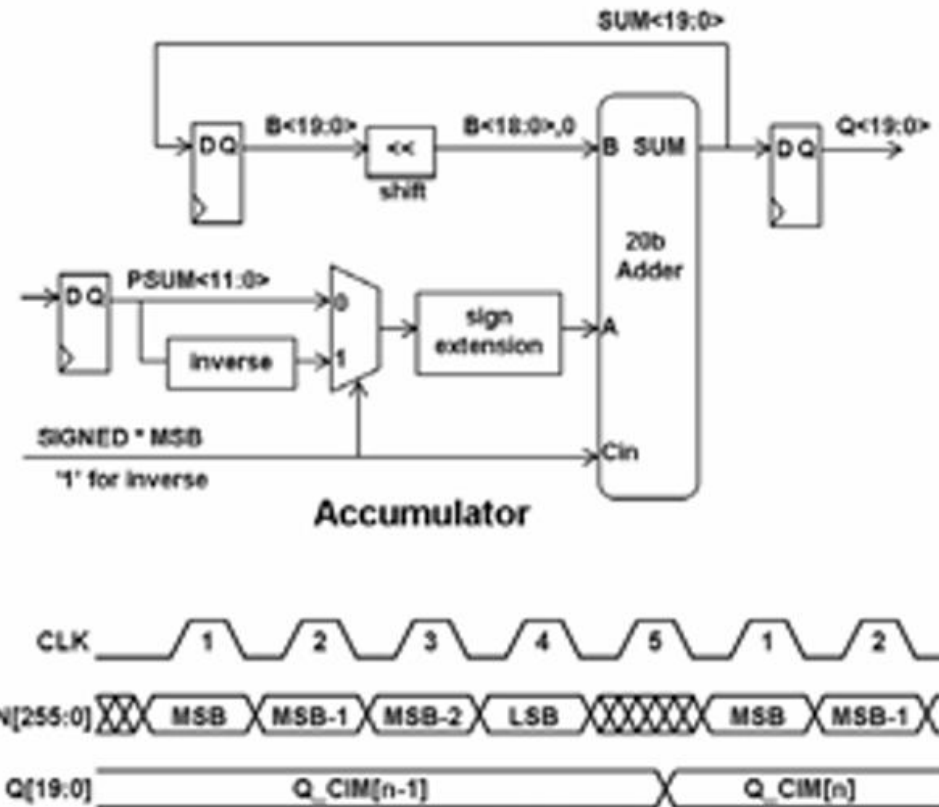■ Require 5 cycles for 4-bit input activation



Structure


- Dynamic voltage scaling

- 0.8V for weight updating
- 0.68V for MAC operation
- Better NM and less dynamic power





- Interleaved 28T & 14T Adder

- Lower dynamic power

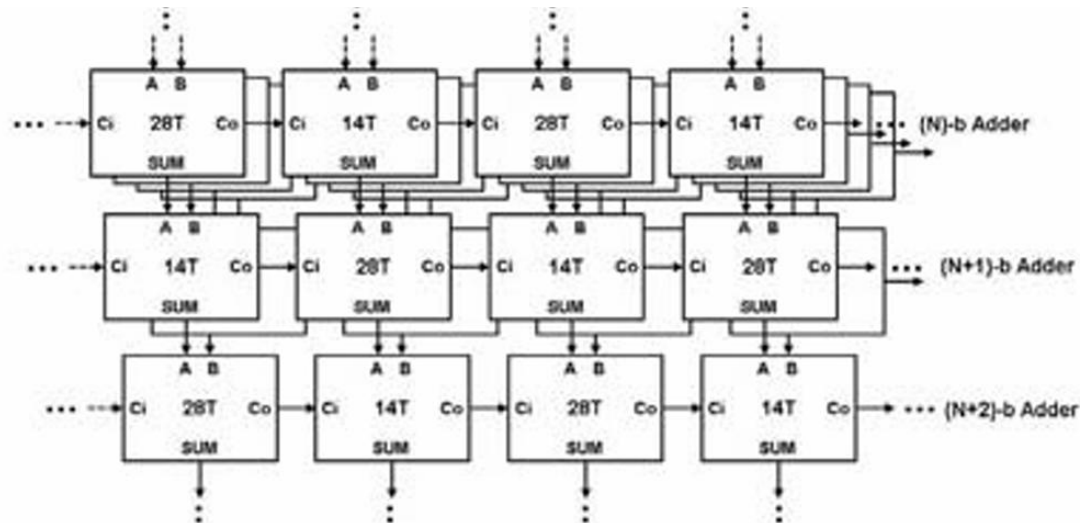




Structure

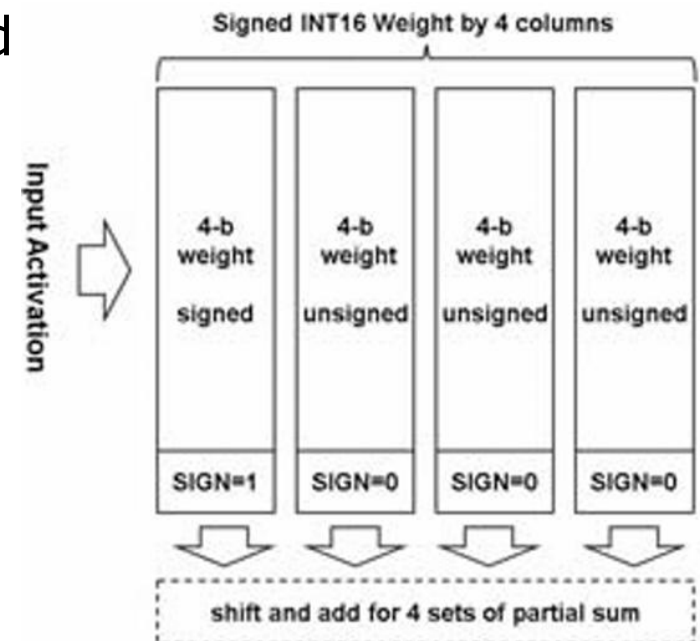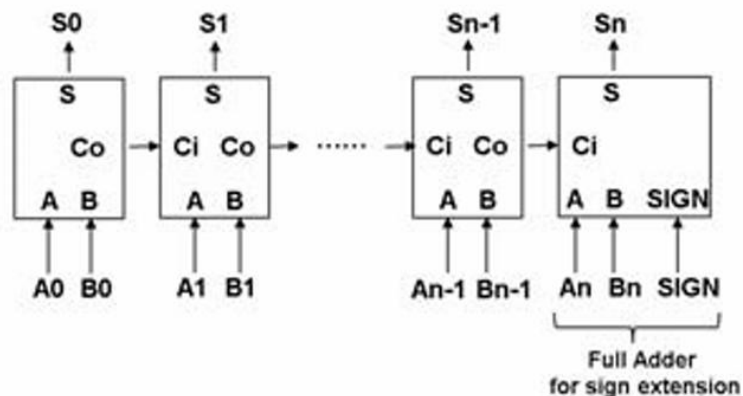- Update weight and perform MAC simultaneously
 - When input = 0, Update weight
- Flexible bit width
 - Separate 16 bit into 4b signed And 3x4b unsigned



Result

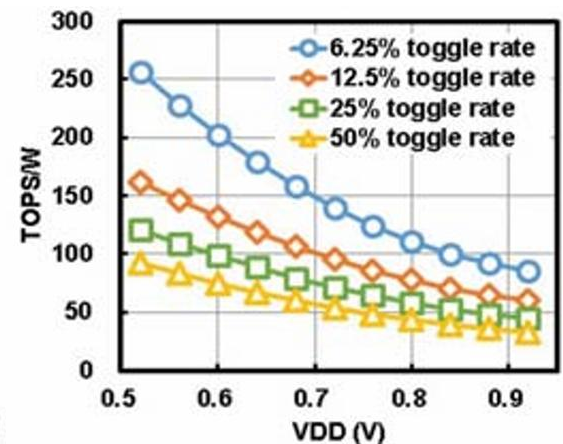  - 89TOPS/W under 0.72V for a sparse pattern
 - (18% input toggle rate, 50% 1s for weights)
- 52TOPS/W for a dense pattern
 - (50% input toggle rate, 50% 1s for weights)
- 3.3TOPS from 0.72V at 25°C
 - TOPS/W and TOPS/area improving by 2.8 \times and 19 \times under 5nm process compared to 22nm design



Conclusion

- Full precision

- Digital adder tree structure with 256×64 bit sram array

- Low power

- Dynamic voltage scaling (lower VDD for MAC)
 - Half of the 28T adders are replaced by 14T adders

- Highly programmable


- Support different input bit-width and weight bit-width
 - Requires extra adder for sign extension and control blocks

2022




Motivation & Background

 - Accuracy and scale of analog approach is limited
 - MOS PVT variation
 - ADC output range under dynamic voltage scaling
 - Truncation and gain error of ADC
 - Nonlinear I_d due to drain-induced-barrier-lowering for current-based approach (lower V_t for short channel)
 - Smaller caps with technology-scaling for cap-approach
 - Analog components are not good for testing



Motivation & Background

 - Digital approach achieves better performance
 - $>1.3\times$ power efficiency
 - $>1.4\times$ performance/area efficiency





Features

- Allows simultaneous MAC and write operations
 - Time is wasted when updating weights
- Small area
- Low power
- Flexible bit width
 - 4b, 8b, ... weight and input



Structure

 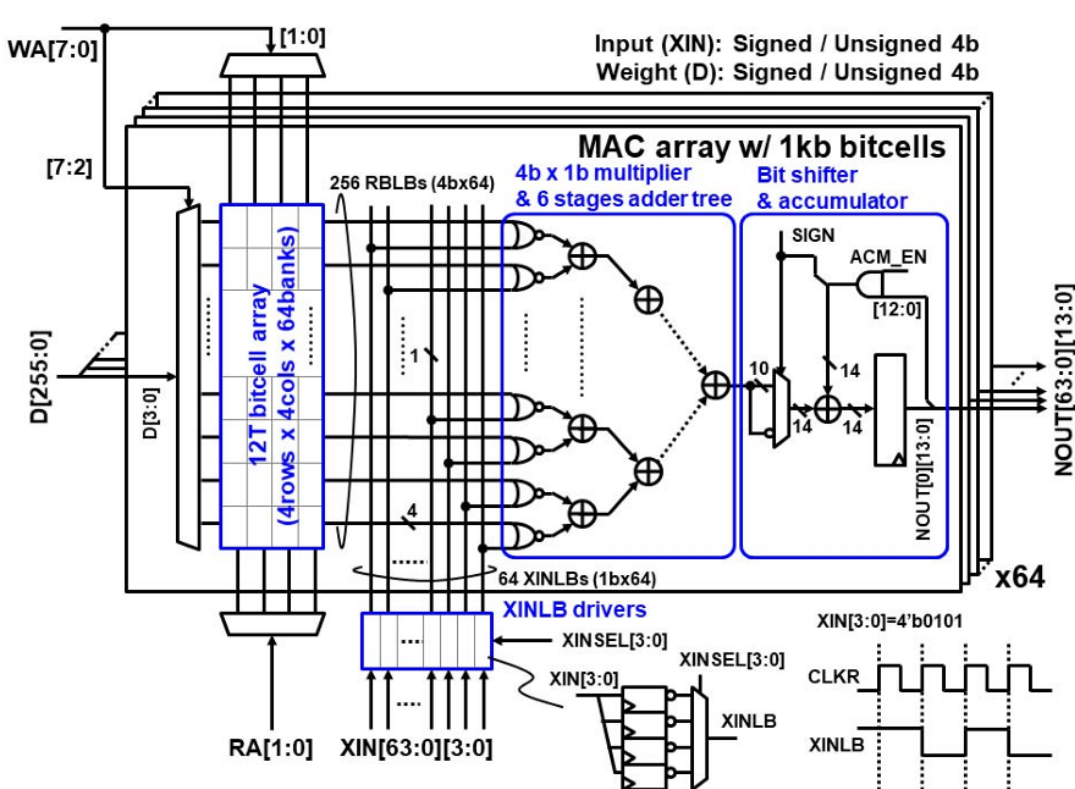- 64 MAC arrays with 64kb of 12T sram cell
- 64 banks, each bank contains 4b×4b
- MAC operation requires 5 clock cycles



Structure

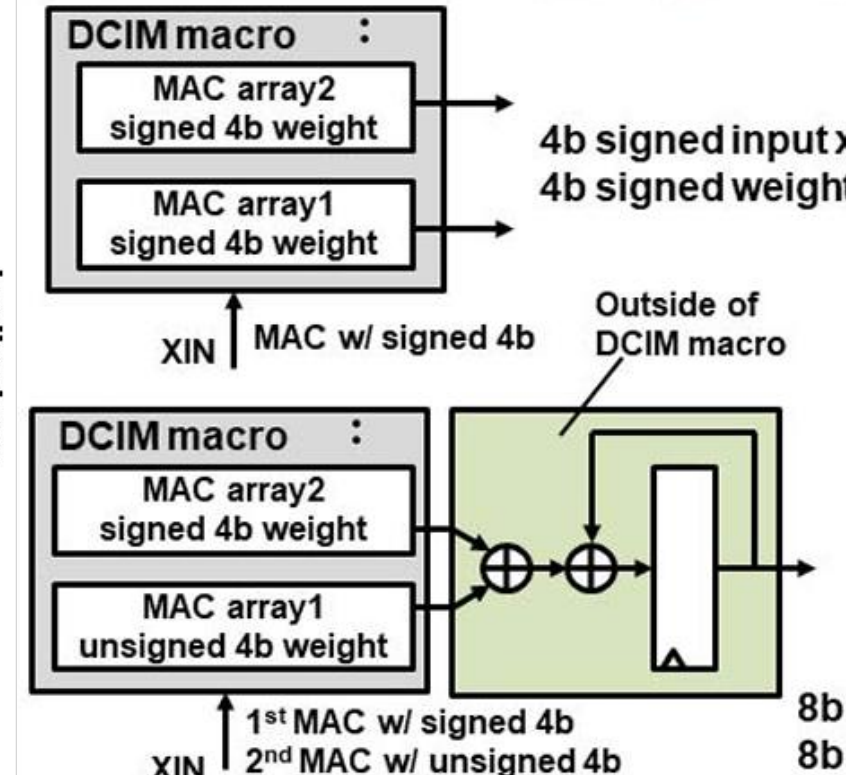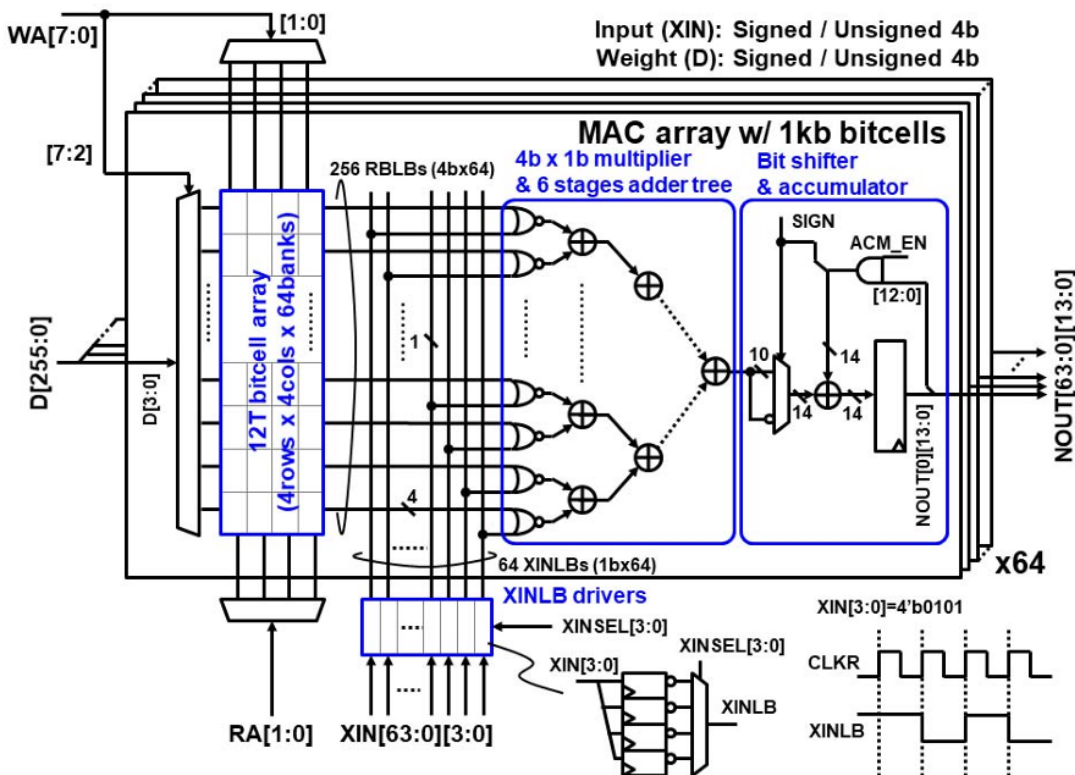
- Read operations reads data from the cell to NOUT
- Accumulator/Adder does sign extension if needed
- Can support 8b data or more



Structure


■ Inverse FA

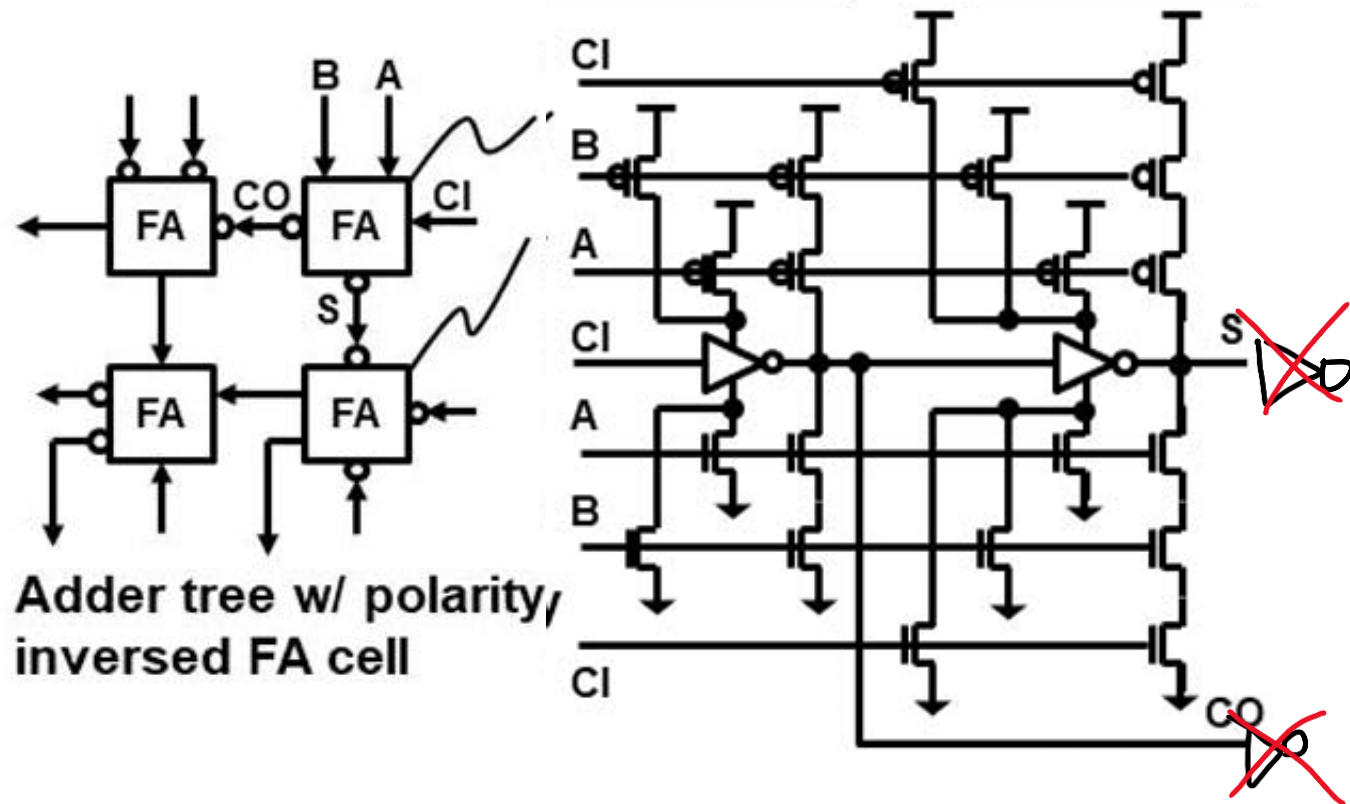- 12.5% smaller area, 15 % less total MAC power
- $FA(\bar{A}, \bar{B}, \bar{C}_{in}) = (\bar{S}, \bar{C}_{out})$





Structure

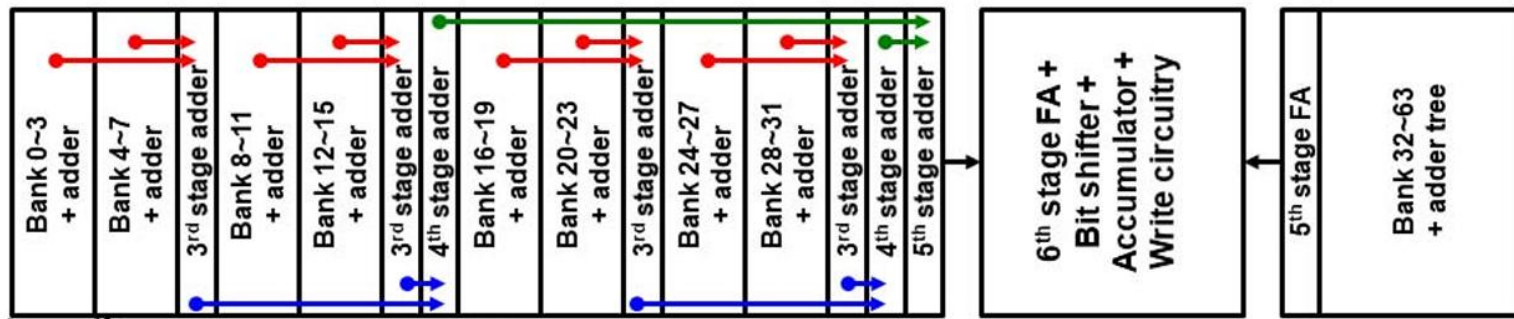- Place adder closer to sram cell
 - Easier for routing
 - Shorter wire
- Merge 12T sram with logic part
 - No dummy space for transition region between sram/add
 - Space can be less than 6T sram design




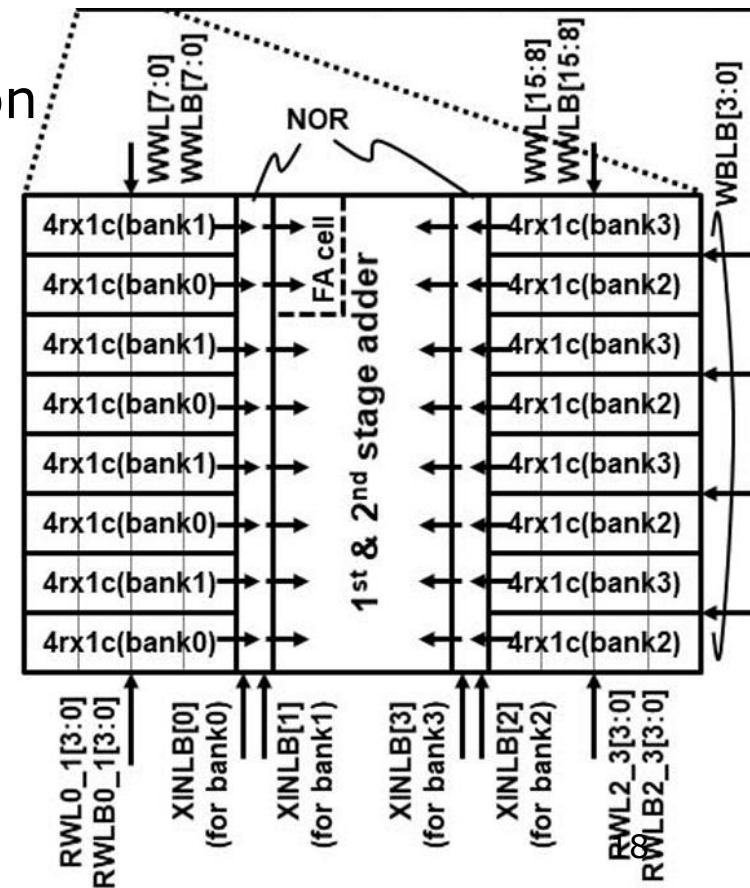 - Interleaved write WL
 - Easier for routing in x-direction
- Shared Read WL
 - Easier for routing in y-direction





Structure

 - No RBL precharge
 - CMOS output of 12 T sram does not need precharge
 - Saves power





Structure

 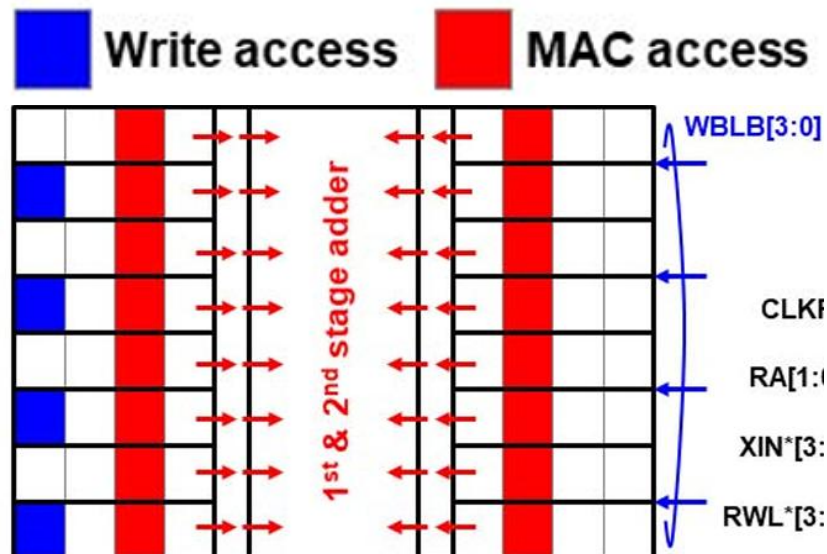- Update weight when MAC is not using the cell
 - Time of updating can be faster than MAC if faster clock for write operation is used



Result

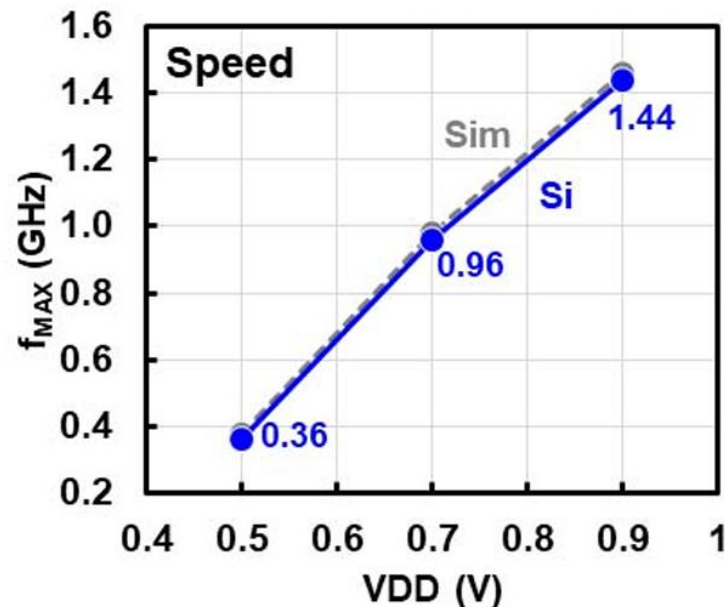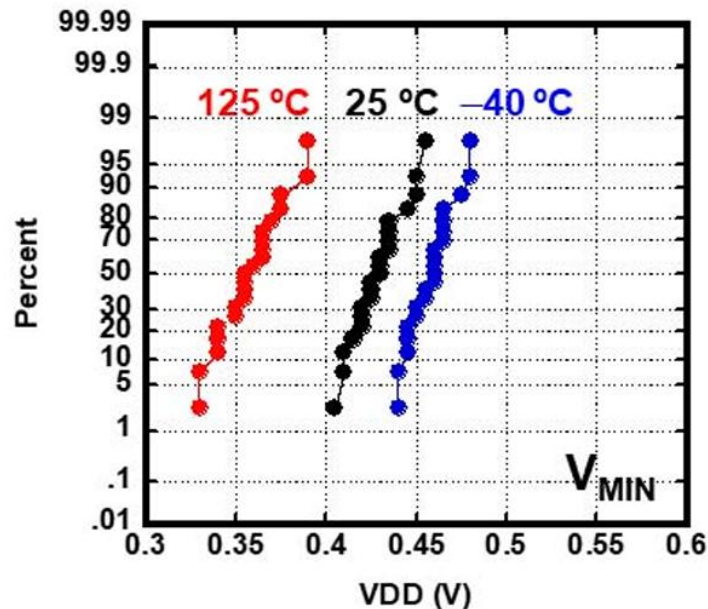- Area: 12208 μm^2
 - 3 \times smaller than using a similar digital architecture
- Vmin: 0.5V at -40°C with a 95% yield.
- Fmax: 0.36, 0.96, 1.44GHz at 0.5, 0.7, 0.9V




Result

■ TOPS/W vs TOPS/mm² chart:

□ VDD = 0.5 V ~ 0.9V

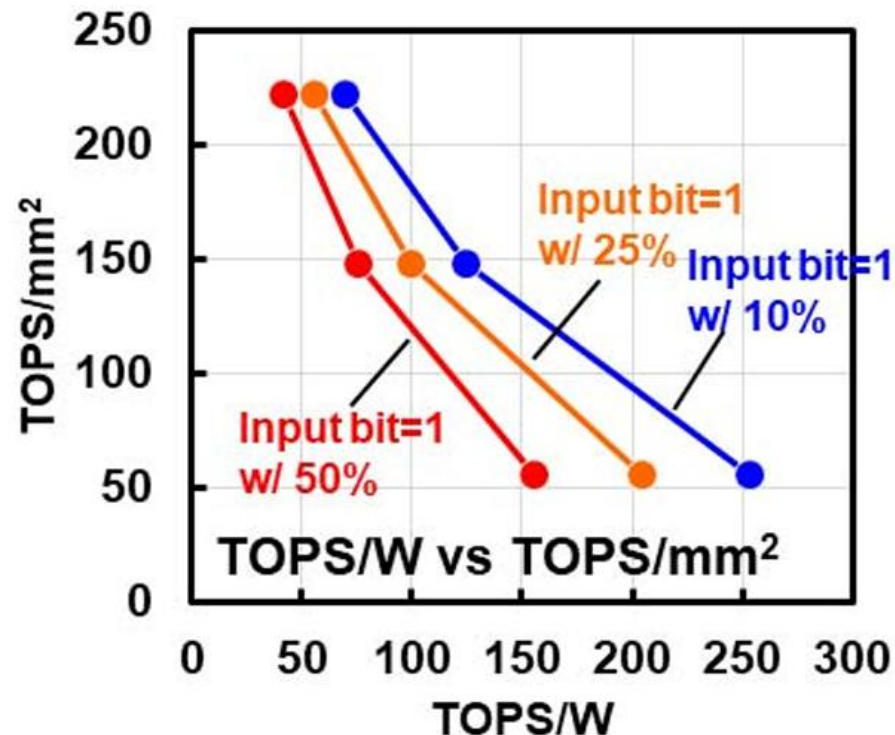□ 253.5, 205.0 and 155.2 TOPS/W with 10, 25 and 50% input bit sparsity under 0.5 V



Conclusion

- Allows simultaneous MAC and write operations
 - Update weight while not used for MAC
 - Use a faster clock for updating
- Small area
 - 12T sram is better than 6T sram
 - Inversed FA
 - Shared WL/ interleaved WL
- Low power
 - 12T sram does not need BL precharge
 - Inversed FA
- Flexible bit width
 - Additional shift and add control